

## RC Circuit Analysis

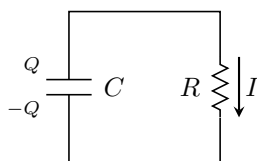


Figure 1: A basic RC circuit.

Consider the elementary RC circuit depicted in Figure 1. We seek to derive an expression for the magnitude of the charge  $Q$  on either plate of the capacitor as a function of time  $t$ , as well as other values from Figure 1 as needed.

To begin, analyze the circuit using Kirchhoff's Voltage Law. According to said law and WLOG<sup>[1]</sup>, analyze the circuit in a clockwise direction beginning in the bottom-left corner as indicated by Figure 1. This analysis will yield the following equation, where  $V_C$  is the voltage gain across the capacitor and  $V_R$  is the voltage drop across the resistor.

$$V_C - V_R = 0$$

Let's express  $V_C$  and  $V_R$  in terms of other variables from Figure 1. Notably,  $V_C$  can be related to  $C$  and  $Q$  through the definition of capacitance and  $V_R$  can be related to  $I$  and  $R$  via Ohm's Law, as shown in Figure 2.

$$\begin{array}{ccc}
 C = \frac{Q}{V_C} & & \\
 V_C = \frac{Q}{C} & & V_R = IR \\
 \swarrow & & \searrow \\
 \frac{Q}{C} - IR = 0
 \end{array}$$

Figure 2: Introducing more variables into the circuit analysis.

We still need to find a way to introduce time. Fortunately, current is the time derivative of charge. While it might seem natural to substitute  $\frac{dQ}{dt}$  for  $I$ , this will actually lead to an incorrect answer — current is the rate at which charge  $q$  passes through the circuit<sup>[2]</sup>, not the rate of change of the magnitude of charge  $Q$  on the plates of the capacitor. While it may now be tempting to substitute  $\frac{dq}{dt}$  for  $I$  and dismiss any relationship between  $q$  and  $Q$ , the pair are intrinsically related.

In order to proceed, we must relate  $q$  to  $Q$ . Let  $\Delta q$  be a small quantity of charge that leaves the positive plate, passes through the circuit, and ends up on the negative plate. When  $\Delta q$  leaves the positive plate,  $Q$  decreases by  $\Delta q$ ; in other words, the change in  $Q$ ,  $\Delta Q$ , is equal to  $-\Delta q$ , or  $\Delta Q = -\Delta q$ . This is the relationship that we were looking for.

<sup>1</sup>"Without the Loss Of Generality"

<sup>2</sup>Or, more formally, a cross section of it.

Both sides of the relationship  $\Delta Q = -\Delta q$  can be differentiated with respect to time to relate said expression back to current  $I$ , as follows.

$$\begin{aligned}\Delta Q &= -\Delta q \\ \frac{dQ}{dt} &= -\frac{dq}{dt} \\ \frac{dQ}{dt} &= -I \\ I &= -\frac{dQ}{dt}\end{aligned}$$

Substitute the above definition of current into the resultant equation from Figure 2.

$$\frac{Q}{C} + \frac{dQ}{dt} R = 0$$

Solve the above first-order differential equation for  $Q$ , as follows. Note that  $Q_0$  is the initial charge on the plates at time  $t = 0$ , while  $Q$  is the variable charge on the plates at time  $t$ .

$$\begin{aligned}\frac{Q}{RC} + \frac{dQ}{dt} &= 0 \\ \frac{dQ}{dt} &= -\frac{Q}{RC} \\ \frac{dQ}{Q} &= -\frac{1}{RC} dt \\ \int_{Q_0}^Q \frac{1}{Q} dQ &= \int_0^t -\frac{1}{RC} dt \\ [\ln(Q)]_{Q_0}^Q &= \left[ -\frac{t}{RC} \right]_0^t \\ \ln(Q) - \ln(Q_0) &= -\frac{t}{RC} \\ \ln\left(\frac{Q}{Q_0}\right) &= -\frac{t}{RC} \\ \frac{Q}{Q_0} &= e^{-\frac{t}{RC}} \\ \boxed{Q} &= \boxed{Q_0 e^{-\frac{t}{RC}}}\end{aligned}$$

Note that the above equation can be holds true for  $V$  and  $V_0$ , and  $I$  and  $I_0$ , as well. These can be derived as follows<sup>[3]</sup>.

$$\begin{aligned}\frac{Q}{C} &= \frac{Q_0}{C} e^{-\frac{t}{RC}} & \frac{Q}{RC} &= \frac{Q_0}{RC} e^{-\frac{t}{RC}} \\ \boxed{V} &= \boxed{V_0 e^{-\frac{t}{RC}}} & \boxed{I} &= \boxed{I_0 e^{-\frac{t}{RC}}}\end{aligned}$$

---

<sup>3</sup>The substitutions are chosen and made based on the definition of capacitance and Ohm's law.